

# Двухконтактный квантовый интерферометр и процессы в нем.

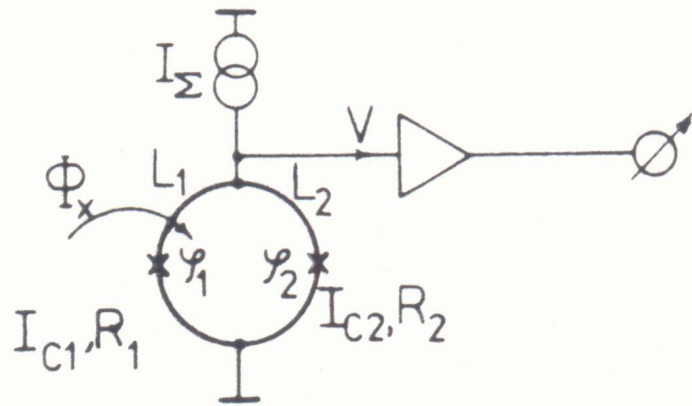


Fig. 7 Basic circuit of a DC SQUID. We assume the junction critical currents  $I_{C1}$ ,  $I_{C2}$  and normal resistances  $R_1$ ,  $R_2$  to be coupled with a relation  $I_{C1} R_1 = I_{C2} R_2 = V_C$ .

## RSJ -модель

$$\bar{V}_1 = \bar{V}_2 = \bar{V}$$

$$\varphi_1 - \varphi_2 = \frac{2\pi}{\Phi_0} \Phi$$

$$\Phi = \Phi_x - L_1 I_1 + L_2 I_2$$

$$I_\Sigma = I_1 + I_2$$

$$I_1 = I_{C1} \sin \varphi_1 + \frac{\Phi_0}{2\pi R_1} \varphi_1 + C_1 \frac{\Phi_0}{2\pi} \ddot{\varphi}_1 + \tilde{I}_{f1}$$

$$I_2 = I_{C2} \sin \varphi_2 + \frac{\Phi_0}{2\pi R_2} \varphi_2 + C_2 \frac{\Phi_0}{2\pi} \ddot{\varphi}_2 + \tilde{I}_{f2}$$

# Двухконтактный квантовый интерферометр S- состояние

$$\Psi = \varphi_1 + \eta = \varphi_2 - \varphi_e + \eta$$


$$\operatorname{tg} \eta = \frac{I_{C2} \sin \varphi_e}{I_{C1} + I_{C2} \cos \varphi_e}$$

$$\overline{\Phi}_{1,2} = \overline{\Phi}_{1,2} = 0, \quad \overline{V} = 0, \quad I_1 < I_{C1}, \quad I_2 < I_{C2}$$

$$\varphi = \varphi_1 - \varphi_2 = \varphi_e - \frac{2\pi}{\Phi_0} (L_1 + L_2)(L_1 I_1 - L_2 I_2) / (L_1 + L_2)$$

$$\varphi = \varphi_x - L_+ I_L \frac{2\pi}{\Phi_0}$$
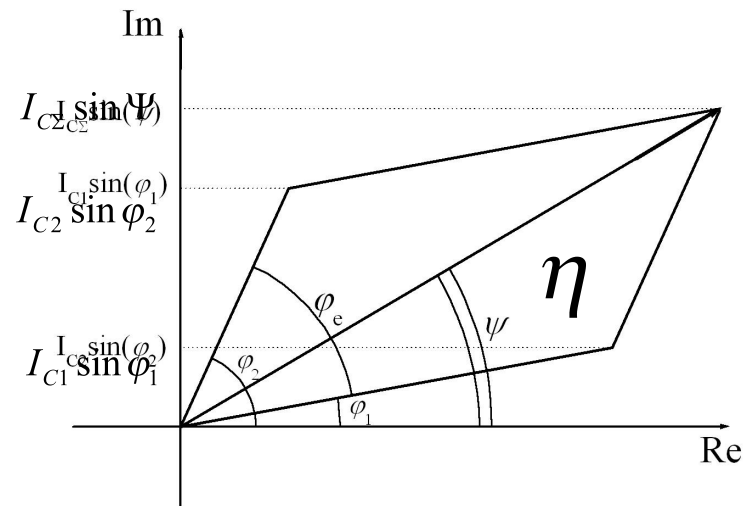
$$I_L = (L_1 I_1 - L_2 I_2) / (L_1 + L_2)$$



$$L_1 I_{C1} \ll \Phi_0, \quad L_2 I_{C2} \ll \Phi_0$$

$$\varphi = \varphi_1 - \varphi_2 \approx \varphi_e$$

$$I_\Sigma = I_1 + I_2 = I_{C1} \sin \varphi_1 + I_{C2} \sin \varphi_2$$


$$I_1 = I_\Sigma \frac{L_2}{L_+} + I_L$$

$$I_2 = I_\Sigma \frac{L_1}{L_+} - I_L$$

$$2I_L = I_1 - I_2 + I_\Sigma (L_1 - L_2) / (L_1 + L_2)$$

$$I_L = \frac{I_{c1}^2 - I_{c2}^2}{2I_{C\Sigma}} \sin \psi + \frac{I_{c1} I_{c2}}{I_{C\Sigma}} \cos \psi \sin \varphi_X + \frac{L_1 - L_2}{2L_+} I_\Sigma$$
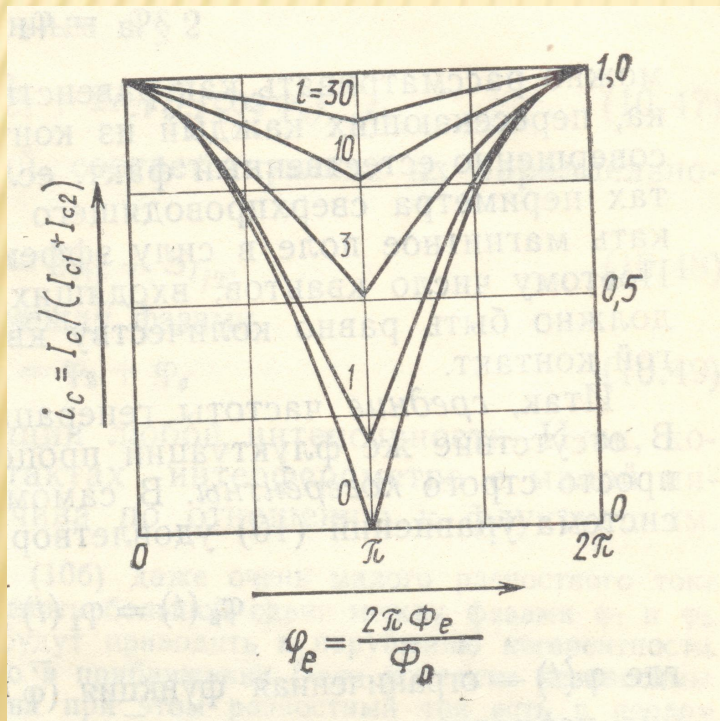
$$I_{C\Sigma} = I_{C\Sigma} (I_{c1} / I_{c+}, \varphi_X) = (I_{C1}^2 + I_{C2}^2 + 2I_{C1} I_{C2} \cos \varphi_X)^{1/2}$$





$$(I_{CM})_{\max} = I_{c1} + I_{c2}$$

$$(\varphi_e = 0, 2\pi n)$$

$$(I_{CM})_{\min} = |I_{c1} - I_{c2}|$$

$$(\varphi_e = \pi, \dots)$$
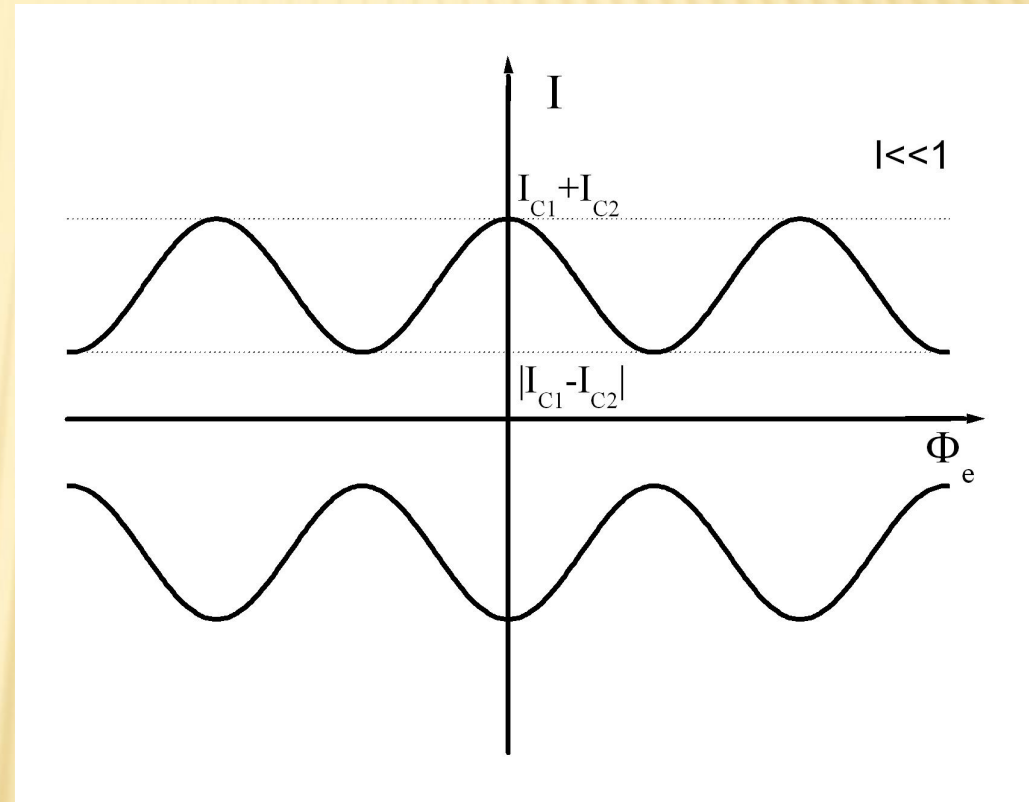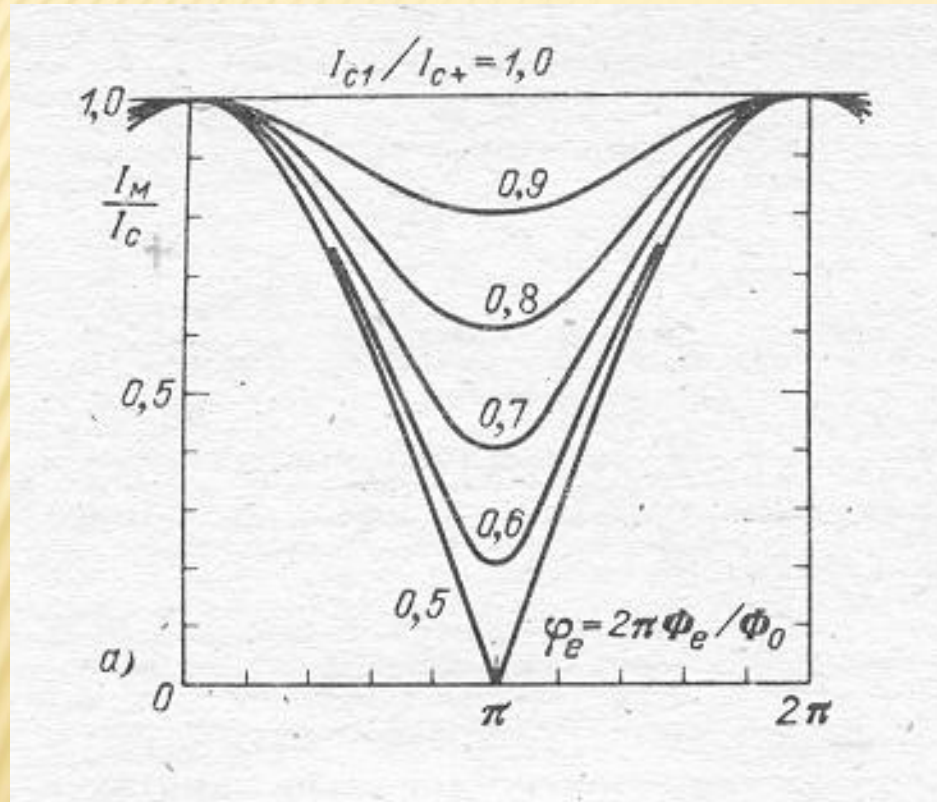
# Двухконтактный квантовый интерферометр S- состояние



S-Состояния,  $L_1 I_{C1} \gg 1, L_2 I_{C2} \gg 1$

$$\varphi_1 - \varphi_2 = \varphi \approx 2\pi n + \varphi_e \quad \varphi_e \ll \pi$$

$$\varphi_e = \frac{2\pi}{\Phi_0} (\Phi_e - n\Phi_0) = 2\pi \frac{\Phi_e}{\Phi_0}$$

$$\phi = \phi_e - \frac{2\pi}{\Phi_0} L_+ I_L \Rightarrow I_L = \frac{\Phi'_e}{L_+}$$

$$I_1 = \frac{L_2}{L_+} I_\Sigma + \frac{\Phi'_e}{L_+}$$

$$I_2 = \frac{L_1}{L_+} I_\Sigma - \frac{\Phi'_e}{L_+}$$

Граница S-состояния

$$I_1 = \pm I_{C1}$$

$$I_2 = \pm I_{C2}$$

Допустим


$$n = 0, \Phi'_e = \Phi_e$$

$$I_{\Sigma 1} = \frac{L_+}{L_2} I_{C1} - \frac{\Phi'_e}{L_2}$$

$$I_{\Sigma 2} = -\frac{L_+}{L_2} I_{C1} - \frac{\Phi'_e}{L_2}$$

$$I_{\Sigma 3} = \frac{L_+}{L_1} I_{C2} + \frac{\Phi'_e}{L_1}$$
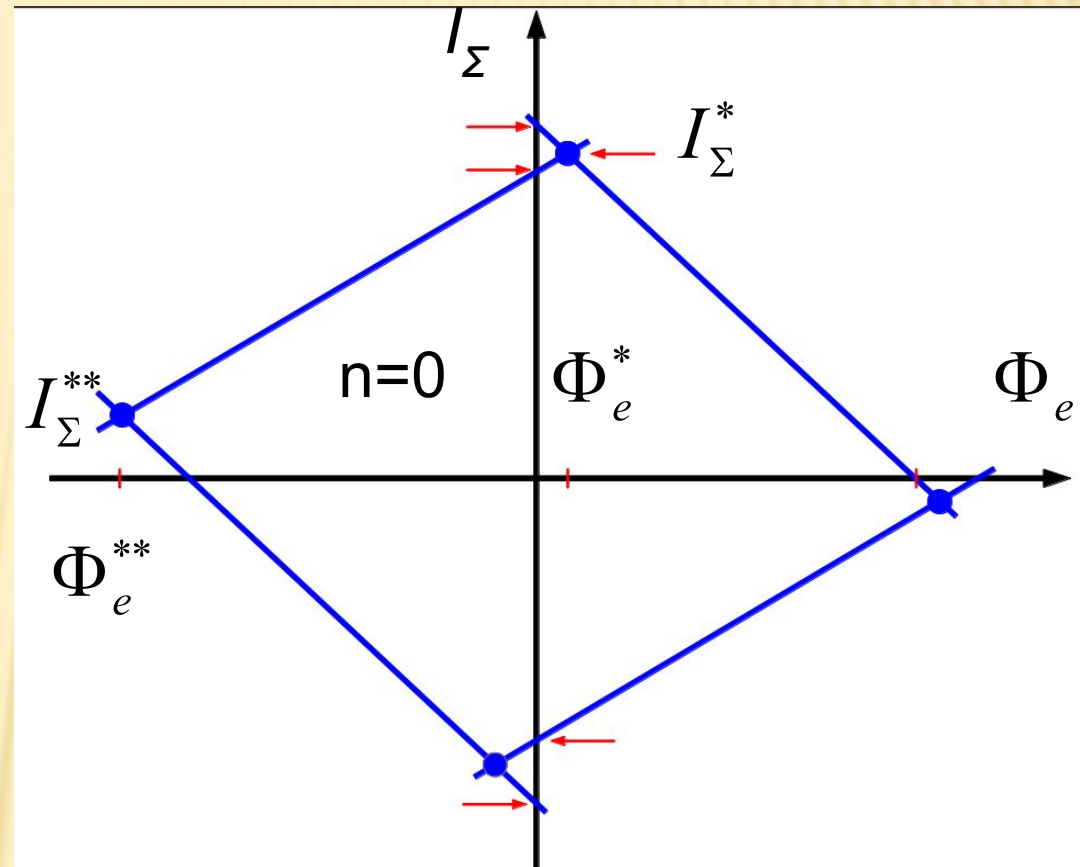
$$I_{\Sigma 4} = -\frac{L_+}{L_1} I_{C2} + \frac{\Phi'_e}{L_1}$$




Характерные точки: 1)  $I_{C\text{MAX}}$  определяется из условия  $I_{\Sigma 1} = I_{\Sigma 3}$

$$I_{\Sigma}^* = \frac{L_+}{L_2} I_{C1} - \frac{\Phi_e}{L_2} = \frac{L_+}{L_1} I_{C2} + \frac{\Phi_e}{L_1} \Rightarrow I_{\Sigma}^* = I_{C1} + I_{C2} \quad \Phi_e^* = L_2 I_{C2} - L_1 I_{C1}$$

$$I_{\Sigma}^{**} = I_{C2} - I_{C1} \quad \Phi_e^{**} = -(L_2 I_{C2} + L_1 I_{C1}) \gg \Phi_0$$

$$I_{C_{\Sigma}} \approx I_{C+} - \min[\tilde{\Phi} / L_2; (\Phi_0 - \tilde{\Phi}) / L_1]$$
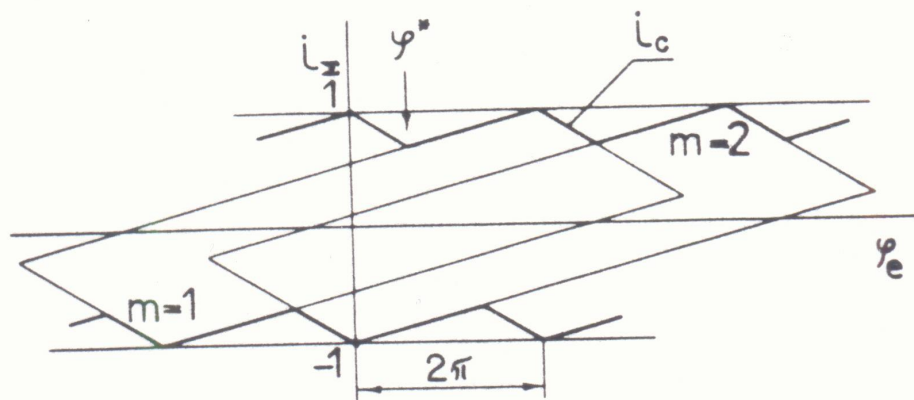
$$\Phi_e = \Phi_e - (L_1 I_{C1} - L_2 I_{C2}) - n\Phi_0$$



$$\Delta I_{C\Sigma} \approx \Phi_0 / L_+$$

QUID. Fig. 8 Regions corresponding to various numbers of magnetic flux quanta stored in the double-junction interferometer, at  $\mathcal{L} \gg 1$ . For large but finite  $\mathcal{L}$ , the tops of the parallelograms are rounded - see <sup>24</sup> for the analytical description.

# Двухконтактный квантовый интерферометр. Потенциальная энергия.

Зависимость  $\Phi(\Phi_e)$  в S-состоянии.

$$I_{\Sigma} = 0$$

$$U(\varphi_1, \varphi_2) = \frac{I_{C1}\Phi_0}{2\pi}(1 - \cos \varphi_1) + \frac{I_{C2}\Phi_0}{2\pi}(1 - \cos \varphi_2) + \frac{1}{2L_+} \left[ \frac{\Phi_0}{2\pi}(\varphi_1 - \varphi_2) - \Phi_e - n\Phi_0 \right]^2$$

Стационарное состояние:

$$\frac{\partial U}{\partial \varphi_1} = \frac{\partial U}{\partial \varphi_2} = 0$$

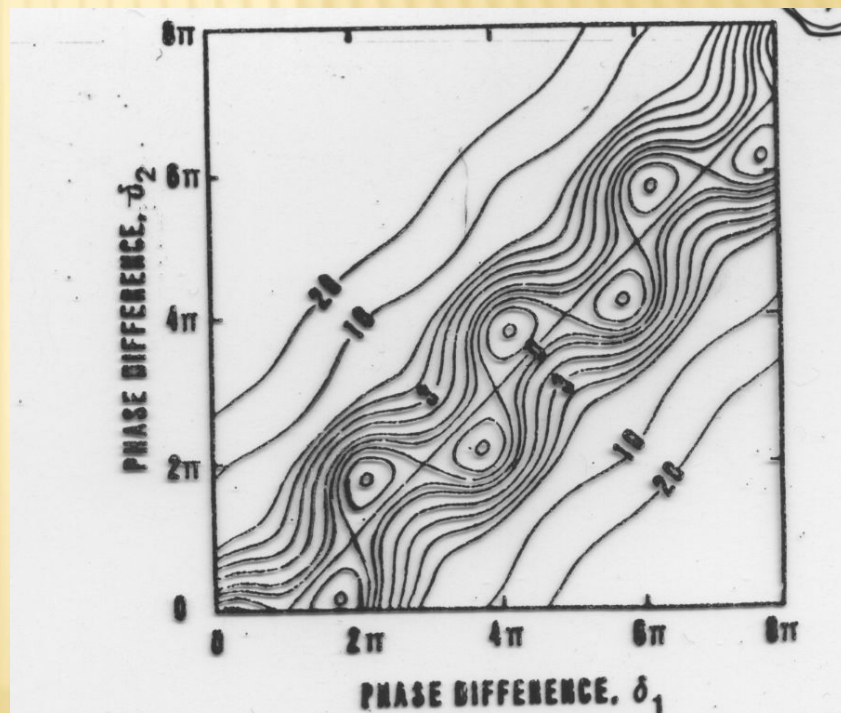


Fig. 1: Contour plot of potential energy as a function of  $\delta_1$  and  $\delta_2$  for  $i = 0$ ,  $\psi = 0.5$  and  $\beta = 1$ .



5

$$I_M \approx I_{ct} - \min \left[ \tilde{\Phi}_e / L_2 ; (\Phi_0 - \tilde{\Phi}_e) / L_1 \right]$$

$$\tilde{\Phi}_e = \Phi_e - (L_1 I_{c1} - L_2 I_{c2}) - 2\pi \Phi_0$$

3

Потенциальная энергия и зависимость  $\Phi(\Phi_e)$  в S-состоянии.

при  $I_e = 0$  !

$$U(\varphi_1, \varphi_2) = \frac{I_{c1} \Phi_0}{2\pi} (1 - \cos \varphi_1) + \frac{I_{c2} \Phi_0}{2\pi} (1 - \cos \varphi_2) + \frac{1}{2L} \left[ \frac{\Phi_0}{2\pi} (\varphi_1 - \varphi_2) - \Phi_e - n\Phi_0 \right]^2$$

Стан. состояние :  $\frac{\partial U}{\partial \varphi_1} = \frac{\partial U}{\partial \varphi_2} = 0$

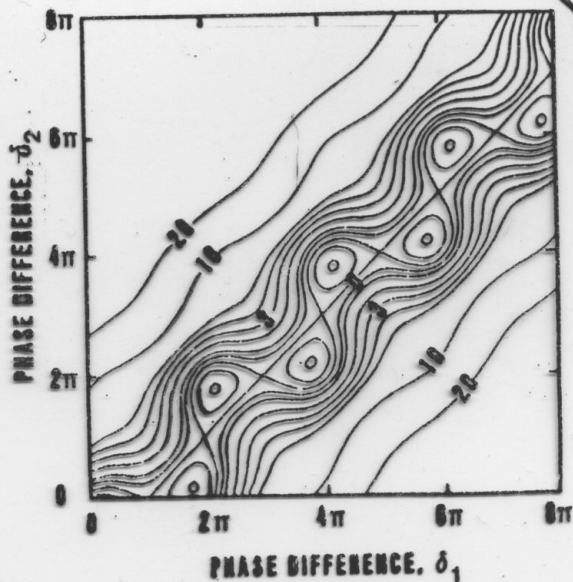


Fig. 1: Contour plot of potential energy as a function of  $\delta_1$  and  $\delta_2$  for  $i = 0$ ,  $\psi = 0.5$  and  $\beta = 1$ .

$$(1) \quad \frac{\Phi_0}{2\pi} (\varphi_1 - \varphi_2) = \Phi_e - L I_{c1} \sin \varphi_1 + \psi \Phi_0 = \Phi_e + L I_{c2} \sin \varphi_2 + \psi \Phi_0$$

Состояние при  $I_e \equiv 0$  дает также:

$$(2) \quad I_{c1} \sin \varphi_1 + I_{c2} \sin \varphi_2 = 0$$

a)  $I_{c2} \gg I_{c1}$ ,  $\varphi_2 \approx k\pi$        $\varphi \approx \varphi_1 - k\pi$

$$\varphi = \varphi_c - \frac{2\pi L I_{c1} \sin \varphi}{\Phi_0} (-1)^k$$

b)  $I_{c1} \approx I_{c2}$ ;      Условие минимума  $U(\varphi_1, \varphi_2)$ :

$$(3) \quad \frac{\partial^2 U(\varphi_1, \varphi_2)}{\partial \varphi_1^2} > 0; \quad \frac{\partial^2 U}{\partial \varphi_2^2} > 0; \quad \left( \frac{\partial^2 U}{\partial \varphi_1^2} \right) \left( \frac{\partial^2 U}{\partial \varphi_2^2} \right) - \left( \frac{\partial^2 U}{\partial \varphi_1 \partial \varphi_2} \right)^2 > 0$$

Пусть  $I_{c1} = I_{c2} = I_c$

(6)

$u_3(2) : \varphi_1 = -\varphi_2 + k \cdot 2\pi$

$u_3(3) \quad \cos \varphi_1 > 0.$

$$\boxed{\frac{\Phi_0}{2\pi} (2\varphi_1) = \Phi_e - L I_c \sin \varphi_2 + n' \Phi_0} \quad \text{или}$$

$$\Phi = \Phi_e - L I_c \sin \pi \left( \frac{\Phi}{\Phi_0} + n' \right) = \Phi_e \mp L I_c \sin \left( \pi \frac{\Phi}{\Phi_0} \right)$$

Период  $\Delta \Phi = 2\Phi_0 \quad (\Delta \varphi = 4\pi);$

$n'$  - четное знак -  
 $n'$  - нечетное = "+"

$\cos \varphi_1 > 0 \quad \text{если} \quad 2k - \frac{1}{2} < \frac{\Phi}{\Phi_0} + n' < 2k + \frac{1}{2}$

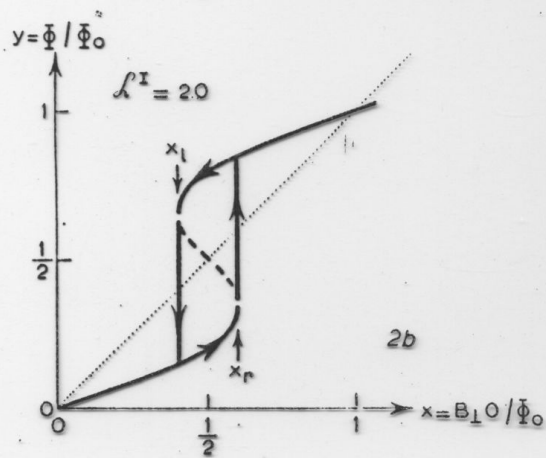
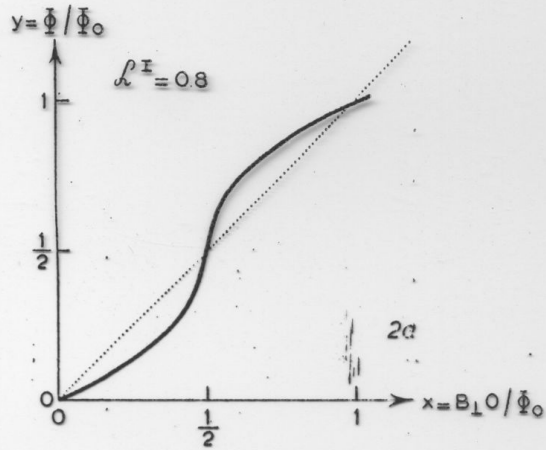


Fig. 2. a) The reduced total embraced magnetic flux  $y \equiv \Phi/\Phi_0$  inside a ring, containing one weak link, is plotted as a function of the reduced applied magnetic flux  $x \equiv B_{\perp 0}/\Phi_0$  for  $\mathcal{L}^I = 0.8$ . b)  $y(x)$  dependence for  $\mathcal{L}^I = 2$ . Flux jumps will occur where the function  $y(x)$  is reentrant as is indicated by arrows at  $y = 1/2\pi \arccos(\epsilon \mp 1/\mathcal{L}^I)$ .

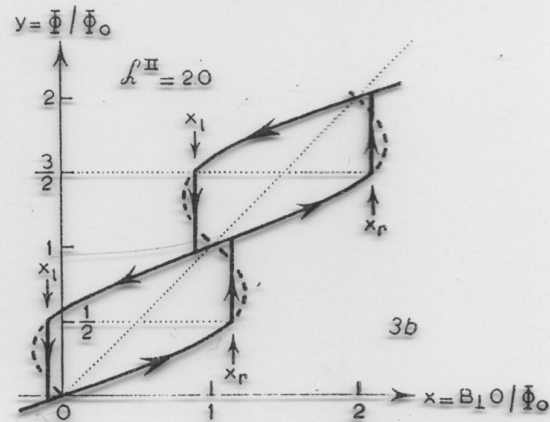
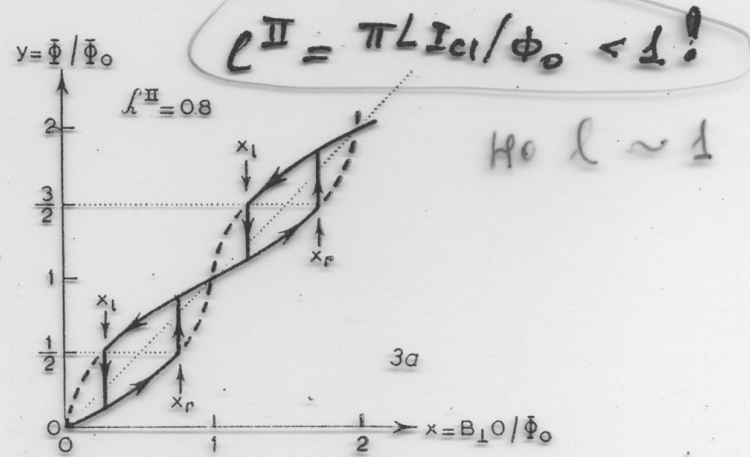


Fig. 3. a) The reduced total embraced magnetic flux  $y \equiv \Phi/\Phi_0$  inside a ring, containing two symmetrical weak links, is plotted as a function of the reduced applied magnetic flux  $x \equiv B_{\perp 0}/\Phi_0$  for  $\mathcal{L}^{II} = 0.8$ . b)  $y(x)$  dependence for  $\mathcal{L}^{II} = 2$ . Flux jumps will occur for both cases  $\mathcal{L}^{II} > 1$  and  $\mathcal{L}^{II} < 1$  at  $y = m + \frac{1}{2}$  when  $x = x_R \equiv (m + \frac{1}{2}) + \mathcal{L}^{II}/\pi$  for increasing applied magnetic field, and when  $x = x_L \equiv (m + \frac{1}{2}) - \mathcal{L}^{II}/\pi$  for decreasing applied magnetic field.

# Двухконтактный квантовый интерферометр и процессы в нем.

## Резистивное состояние, $\beta \ll 1$ .

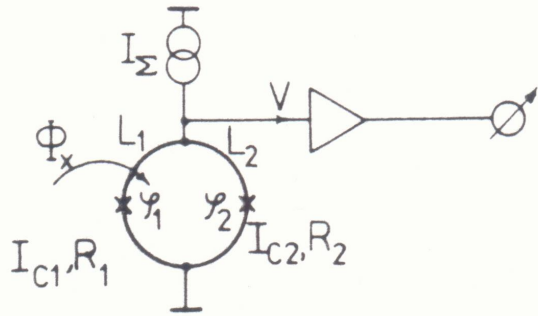


Fig. 7 Basic circuit of a DC SQUID. We assume the junction critical currents  $I_{C1}$ ,  $I_{C2}$  and normal resistances  $R_1$ ,  $R_2$  to be coupled with a relation  $I_{C1} R_1 = I_{C2} R_2 = V_C$ .

$$i_1 + i_2 = i_\Sigma$$

$$l_1 i_1 - l_2 i_2 = \Phi_X > I_M, \quad \bar{V} \neq 0$$

$$l_{1,2} = 2\pi L_{1,2} I_{C+} / \Phi_0; \quad l = l_1 + l_2$$

$$\varphi_X = \bar{\varphi}_X + \tilde{\varphi}_X$$

$$i = \{\varphi_X - (\varphi_1 - \varphi_2)\} / l$$

$$i_{1,2} = i_{C1,2} (\omega_C^{-1} \Psi_{1,2} + \sin \varphi_{1,2} + \tilde{i}_{f1,2})$$

$$s_{i_{f1,2}} = \gamma / (\pi i_{C1,2} \omega_c); \quad \gamma = 2\pi k_B T / I_C \Phi_0$$

$$I_\Sigma > I_M, \quad \bar{V} \neq 0$$

$$l \ll 1; \quad \varphi_1 - \varphi_2 = \varphi_X = \bar{\varphi}_X + \tilde{\varphi}_X$$

$$\omega_C^{-1} \Psi + i_{C\Sigma} \sin \Psi + \tilde{i}_{f+} = i_\Sigma^\otimes$$

$$i_{C\Sigma}^2 = i_{C1}^2 + i_{C2}^2 + 2i_{C1}i_{C2} \cos \bar{\varphi}_X$$

# Двухконтактный квантовый интерферометр и процессы в нем. Резистивное состояние, $\beta \ll 1$ .

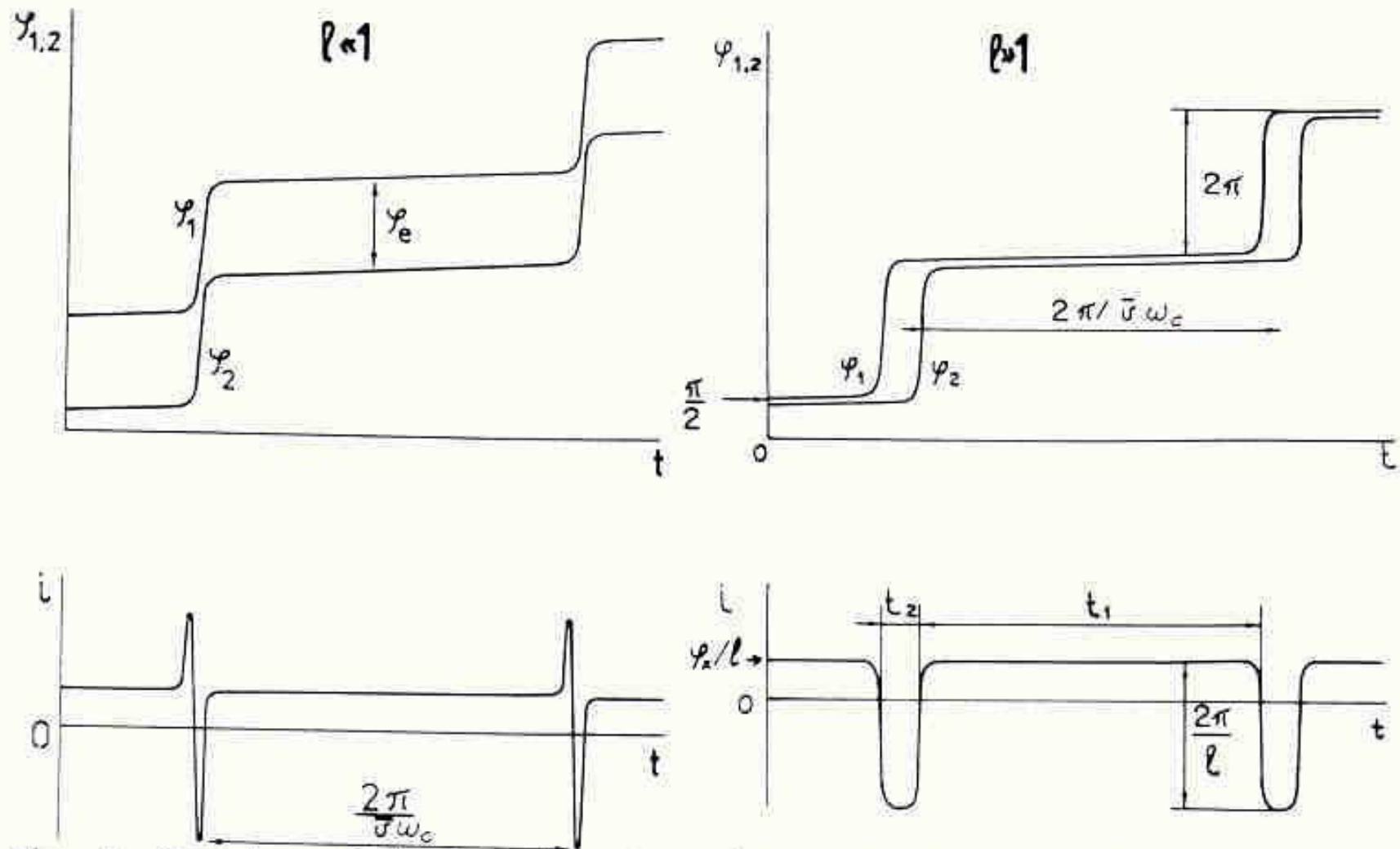



Fig. 9 Dynamics of the Josephson junction phases  $\varphi_{1,2}$  and the circulating current  $i$  in the double-junction interferometer at small (a,  $\beta \ll 1$ ) and large (b,  $\beta \gg 1$ , but  $\bar{v} \ll 1$ ) values of inductance - schematically.

# Двухконтактный квантовый интерферометр и процессы в нем.
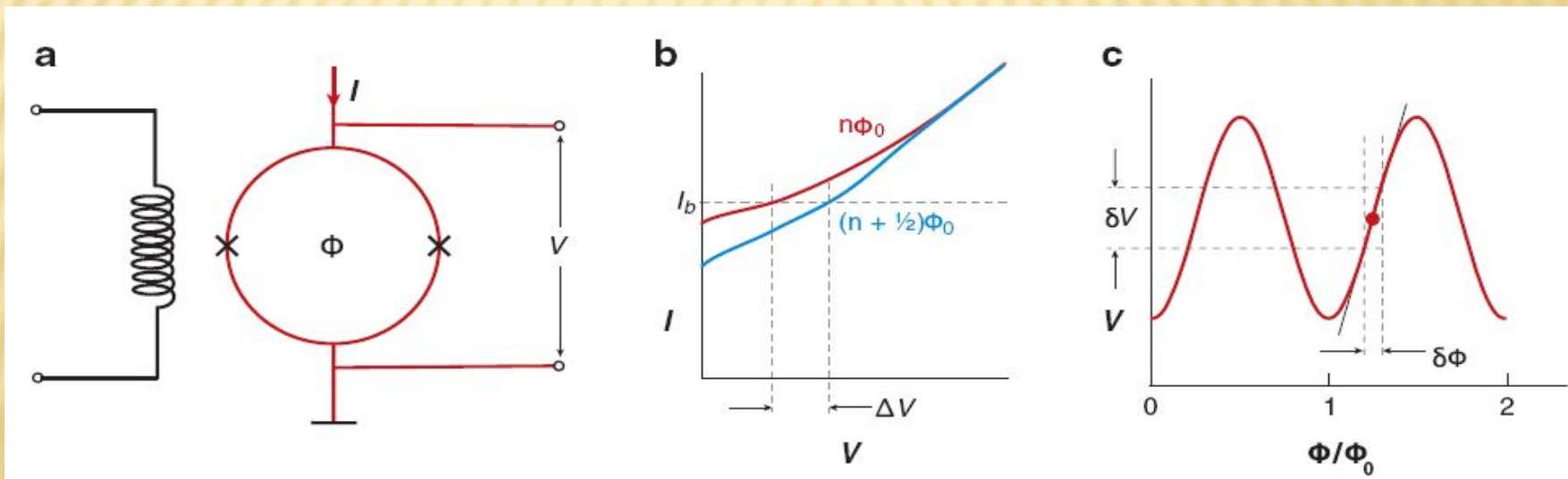
## I. Сигнал и шум отсутствуют. Процессы в рабочей точке

$$i_{\Sigma}^{\otimes} = i_{\Sigma} + \frac{2i_{C1}i_{C2}(i_{C1} - i_{C2})}{\omega_C i_{C\Sigma}^2 (\bar{\varphi}_X)}$$

$$\omega_C^{-1} \Psi = \frac{\bar{U}^2}{i_{\Sigma} - i_{C\Sigma} \cos \Theta}; \quad \omega_C^{-1} \Theta \equiv \bar{U} = [i_{\Sigma}^2 - i_{C\Sigma}^2 (\bar{\varphi}_X)]^{1/2}$$



# Двухконтактный квантовый интерферометр и процессы в нем.

## II. Сигнальные и шумовые характеристики интерферометра

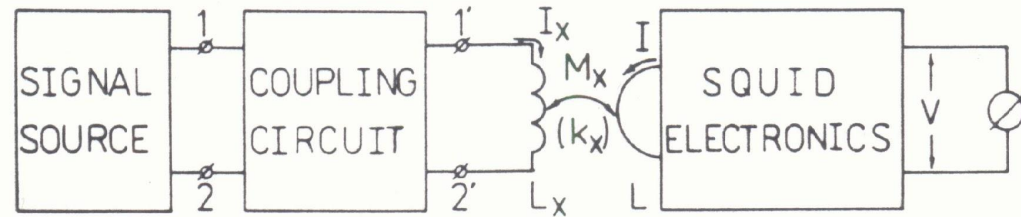


Fig. 1 Basic circuit of signal measurement with a SQUID. Current  $I_x$  applies magnetic flux  $\Phi = M_x I_x$  to the superconducting quantum interferometer, which consists of a superconducting ring with inductance  $L$ , closed with one (for RF SQUID) or two (for DC SQUID) Josephson junctions. Current  $I$  flowing along the interferometer ring induces the back reaction e.m.f.  $E_x = M_x \dot{I}_x$  in the signal coil  $L_x$ , thus acting upon the signal source.

$$\tilde{\Phi}_X = M_X \tilde{I}_X; \quad V = V_N + H \tilde{\Phi}_X$$

$$\hat{I} - \bar{I} = I_N + j\omega Y(\omega) \tilde{\Phi}_X; \quad H = \partial \bar{V} / \partial \Phi_X$$

$$Y(\omega) = \frac{1}{j\omega \mathfrak{Z}_i} + G_i; \quad \Phi_{NV} = V_N / H$$

$$\Phi_{NI} = LI_N \quad \varepsilon_V = \frac{\langle \Phi_{NV}^2 \rangle}{2L\Delta f}$$

$$\varepsilon_I = \frac{\langle \Phi_{NI}^2 \rangle}{2L\Delta f}$$

$$\frac{1}{\mathfrak{Z}_i} = \frac{\partial I}{\partial \Phi_e};$$

$$G_i = \frac{\partial I}{\partial \Phi_X} = \frac{1}{\mathfrak{R}_i}$$



# Двухконтактный квантовый интерферометр и процессы в нем.

## II. Сигнальные и шумовые характеристики интерферометра

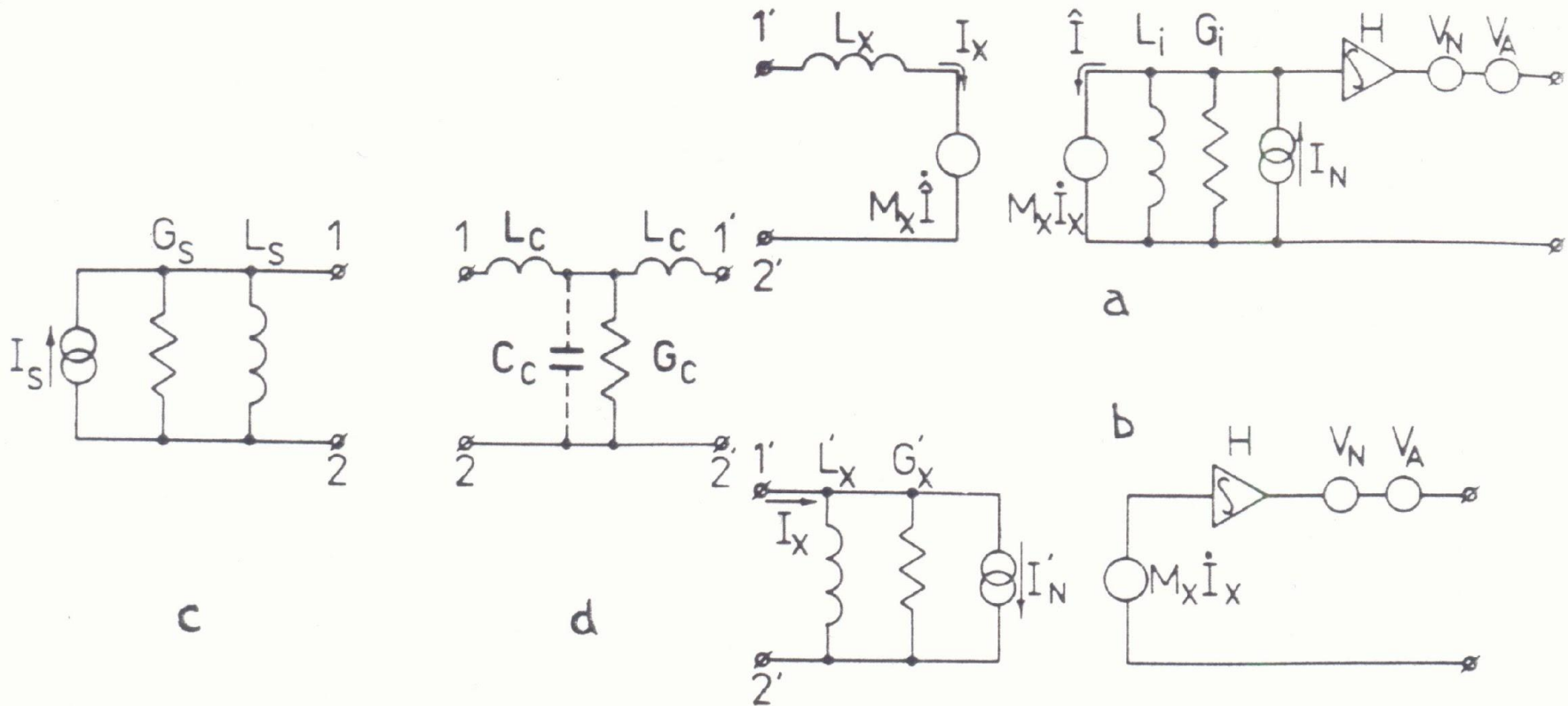


Fig. 10 Equivalent circuits of a SQUID (a,b), a signal source (c) and a coupling circuit (d). Voltage generators  $V_N$  and  $V_A$  describe the SQUID and the amplifier output noise. Integrators reflect the fact that the SQUID output signal  $V = H\Phi_x$  is proportional to  $\Phi_x = \int M_x \dot{I}_x dt$ .

$$H = \frac{\partial \bar{V}}{\partial \bar{\Phi}_X} = \frac{2\pi}{\Phi_0} V_C \frac{\partial \bar{v}}{\partial \varphi_X} = \omega_C \frac{1}{\bar{v}} i_{C1} i_{C2} \sin \bar{\varphi}_X$$

Отклик на шумовое воздействие

$$\Psi + \sin \Psi = \bar{i} + \tilde{i}; \quad \text{нормировки: } \bar{i} = i_{\Sigma} / i_{C\Sigma}; \quad \tilde{i} = i_{f+} / i_{C\Sigma}$$

$$\tilde{i} = \int i_{\omega} e^{j\omega t} d\omega; \quad \hat{\Psi} \equiv \tilde{v} = \int v_{\omega} e^{i\omega t} d\omega$$

Задача: найти  
 $S_{\tilde{v}}(\omega)$  в простейшем случае

$$i_{\omega} = a \cos \omega t; \quad a \ll 1$$

$$\Psi = \Psi_0 + \Psi_1 + \Psi_2 + \dots$$

$$\Psi_k \propto a^k; \quad |\Psi_1| \ll 1$$

$$\hat{\Psi}_k = 0, \quad k > 0$$

$$\sin \Psi = \sin \Psi_0 + \Psi_1 \cos \Psi_0 + \Psi_2 \cos \Psi_0 - \frac{\Psi_1^2}{2} \sin \Psi_0$$

$$\bar{i} = \hat{i}_0 + \hat{i}_1 + \hat{i}_2 + \dots; \quad |\hat{i}_k| \propto a^k$$

$$\Psi_0 + \sin \Psi_0 = \hat{i}_0$$

$$\Psi_1 + \Psi_1 \cos \Psi_0 = \hat{i}_1 + \tilde{i}$$

$$\Psi_2 + \Psi_2 \cos \Psi_0 = \hat{i}_2 + \sin \Psi_0 \frac{\Psi_1^2}{2}$$

Решение уравнения для  $\Psi_0$

$$\hat{i}_0 = \bar{i} - \hat{i}_1 - \hat{i}_2 - \dots$$

$$\Psi_0 = \frac{\bar{v}^2}{\hat{i}_0 - \cos \Theta}; \quad \Theta \equiv \hat{v} \approx \bar{v}$$

$$\hat{v} = \bar{v}^A - \frac{d\bar{v}^A}{d\bar{i}} \hat{i}_1 - \frac{d\bar{v}^A}{d\bar{i}} \hat{i}_2 - \dots$$

Решение уравнения для  $\Psi_1$  это уравнение типа

$$\phi + \tilde{\varphi} \cos \varphi = \tilde{i}; \quad \text{решение:} \quad \tilde{\varphi}(t) = \int_0^t \exp\left\{\int_t^{t'} \cos \varphi dt\right\} \tilde{i}(t') dt'$$

$$\cos \varphi = -\frac{\phi}{\tilde{\varphi}} = -\ln(\phi); \quad \exp\left\{\pm \int \cos \varphi dt\right\} = \text{const} \times \phi^{\pm 1}$$

Поэтому получаем:

$$\tilde{\varphi} = \phi \int \tilde{i}(t') [\phi(t')]^{-1} dt'; \quad \tilde{v} \equiv \tilde{\phi} = \tilde{i} + \phi \int \frac{\tilde{i}(t')}{\phi(t')} dt'$$

Возвращаясь к  $\Psi_k$  видим, что  $\hat{\Psi}_k = 0$  если  $\langle (i_k \varphi_0^{-1}) \rangle = 0$

$$\langle [i_k (i_0 - \cos \Theta)] \rangle \approx \hat{i} \bar{i}_1 - \tilde{i} \cos \Theta + \dots = 0$$

$$\hat{U} = \hat{\Phi} = \bar{U}^A + r_d^A \hat{i}_1 \frac{\langle (\tilde{i} \cos \Theta) \rangle}{\bar{i}}$$

$$\hat{U}_N = \hat{\Phi} = \bar{U}^A + r_d^A \left[ \hat{i}_{f+} - \frac{\langle (\tilde{i}_{f+} \cos \Theta) \rangle}{\bar{i}} \right]$$

$$\Phi_{NV} = \frac{v_N \Phi_0}{h 2\pi} = \frac{\Phi_0}{2\pi i_{c1} i_{c2} \sin \varphi_X} \left[ \hat{i}_{f+} - \frac{\langle (\tilde{i}_{f+} \cos \Theta) \rangle}{\bar{i}} \right]$$

$$S_{i_{f+}} = \frac{\gamma}{\pi i_{c1} \omega_C} + \frac{\gamma}{\pi i_{c2} \omega_C}; \quad \gamma = \frac{2\pi k_B T}{I_{C\Sigma} \Phi_0}$$

$$\varepsilon_V = \frac{\langle \Phi_{NV}^2 \rangle}{2L\Delta f} \approx \frac{12k_B T}{l\omega_C \sin^2(\varphi_X / 2)}$$

Связь со стандартным катушкой?  $k_x^2 \equiv M_x^2 / L_s L_x \ll 1$  (15)


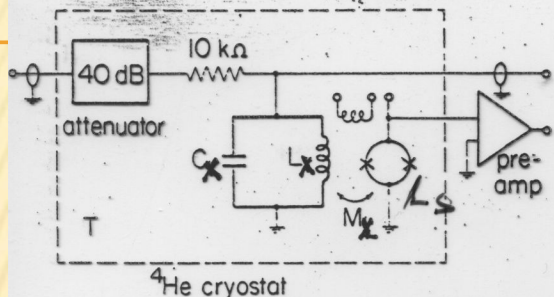


Fig. 9. Experimental configuration for the measurement of the dynamic input impedance of a dc SQUID amplifier.

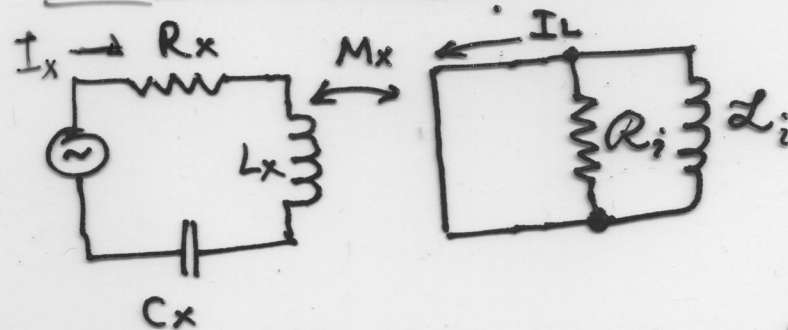

$$Z_T = R_x \left(1 + \frac{L_s k_x^2}{L_i}\right) + \frac{k_x^2 L_s}{R_i C_x} + j\omega \left[ L_x + k_x^2 L_s \left( \frac{R_x}{R_i} - \frac{1}{\omega^2 L_i C_x} \right) \right] + \frac{1}{j\omega C_x}$$

$$\Delta L_x = k_x^2 L_s \left( \frac{R_x}{R_i} - \frac{1}{\omega^2 L_i C_x} \right) = \frac{1}{(2\pi)^2 C_x} \left[ \frac{1}{f_0^2} - \frac{1}{(f_0^0)^2} \right]$$

$$\Delta R_x = k_x^2 L_s \left( \frac{R_x}{R_i} + \frac{1}{R_i C_x} \right) \approx \frac{1}{2\pi C_x} \left[ \left(1 + k_x^2 \frac{L_s}{L_i}\right) \frac{\Delta f}{f_0^2} - \frac{\Delta f^0}{(f_0^0)^2} \right]$$

$$H = \frac{R_i + \Delta R_x}{M_x} \left[ \frac{P(f_0) R_d}{k_B T \Delta f \cdot \eta} \right]^{1/2}$$

$\eta$  - mismatch factor  
 $\Gamma_{dsq} \leftrightarrow 50 \Omega$  cable

Fig. 10. Noise power at resonance  $P(f_0)$  measured at SQUID output, resonant frequency  $f_0$  and width of resonance  $\Delta f$ , as functions of  $\Phi/\Phi_0$  for 20-turn SQUID, at two different temperatures: (a-c)  $T=4.2$  K, (d-f)  $T=1.5$  K. The bias current  $I$  was constant for each set of data: (a)  $I=4.0 \mu\text{A}$ , (b)  $I=5.0 \mu\text{A}$ , (c)  $I=6.0 \mu\text{A}$ , (d)  $I=5.0 \mu\text{A}$ , (e)  $I=6.0 \mu\text{A}$ , (f)  $I=7.0 \mu\text{A}$ . The resonant frequency  $f_0^0$  and bandwidth  $\Delta f^0$  of the unloaded circuit are shown as dashed lines.

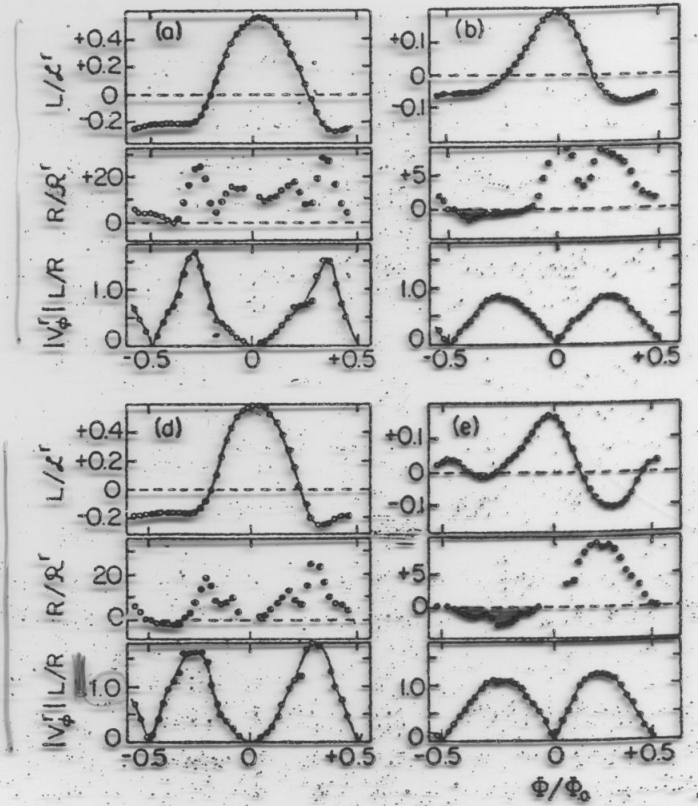
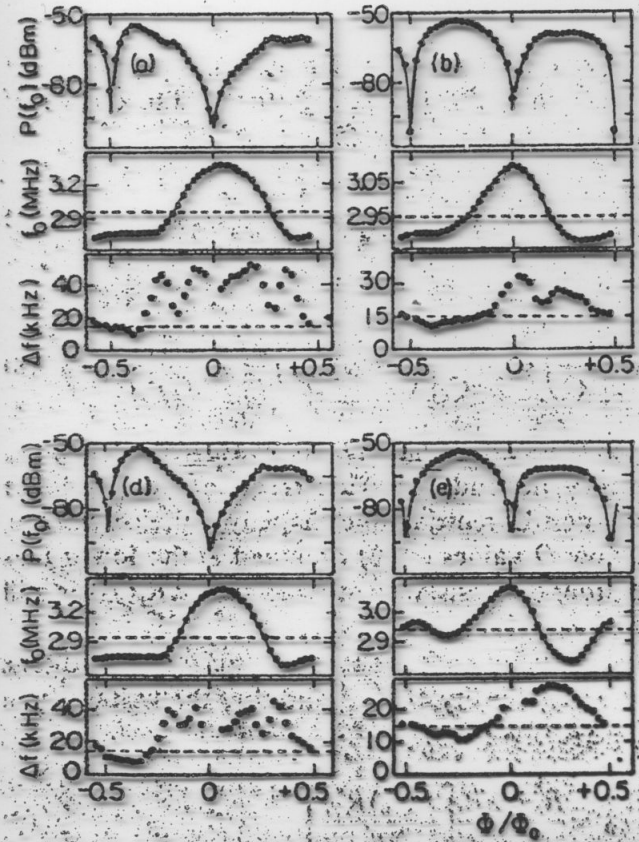


Fig. 11. Dynamic inductance  $L/L^0$ , dynamic resistance  $R/R^0$ , and flux-to-voltage transfer function  $|V_\Phi^0|$  versus  $\Phi/\Phi_0$  obtained from Fig. 10. Note that the scales for  $L/L^0$  and  $R/R^0$  in (a) and (d) differ from those for the remaining figures.