

# The Verilog Language

**These slides were developed by  
Prof. Stephen A. Edwards  
CS dept., Columbia University**

these slides are used for  
educational purposes only

# The Verilog Language

- Originally a modeling language for a very efficient event-driven digital logic simulator
- Later pushed into use as a specification language for logic synthesis
- Now, one of the two most commonly-used languages in digital hardware design (VHDL is the other)
- Virtually every chip (FPGA, ASIC, etc.) is designed in part using one of these two languages
- Combines structural and behavioral modeling styles

# Structural Modeling

- **When Verilog was first developed (1984) most logic simulators operated on netlists**
- **Netlist: list of gates and how they're connected**
- **A natural representation of a digital logic circuit**
  
- **Not the most convenient way to express test benches**

# Behavioral Modeling

- **A much easier way to write testbenches**
- **Also good for more abstract models of circuits**
  - Easier to write
  - Simulates faster
- **More flexible**
- **Provides sequencing**
  
- **Verilog succeeded in part because it allowed both the model and the testbench to be described together**

# How Verilog Is Used

- **Virtually every ASIC is designed using either Verilog or VHDL (a similar language)**
- **Behavioral modeling with some structural elements**
- **“Synthesis subset”**
  - **Can be translated using Synopsys’ Design Compiler or others into a netlist**
- **Design written in Verilog**
- **Simulated to death to check functionality**
- **Synthesized (netlist generated)**
- **Static timing analysis to check timing**

# Two Main Components of Verilog

- **Concurrent, event-triggered processes (behavioral)**
  - *Initial* and *Always* blocks
  - Imperative code that can perform standard data manipulation tasks (assignment, if-then, case)
  - Processes run until they delay for a period of time or wait for a triggering event
- **Structure (Plumbing)**
  - Verilog program build from modules with I/O interfaces
  - Modules may contain instances of other modules
  - Modules contain local signals, etc.
  - Module configuration is static and all run concurrently

# Two Main Data Types

- **Nets represent connections between things**
  - Do not hold their value
  - Take their value from a driver such as a gate or other module
  - Cannot be assigned in an *initial* or *always* block
- **Regs represent data storage**
  - Behave exactly like memory in a computer
  - Hold their value until explicitly assigned in an *initial* or *always* block
  - Never connected to something
  - Can be used to model latches, flip-flops, etc., but do not correspond exactly
  - Shared variables with all their attendant problems

# Discrete-event Simulation

- **Basic idea: only do work when something changes**
- **Centered around an event queue**
  - **Contains events labeled with the simulated time at which they are to be executed**
- **Basic simulation paradigm**
  - **Execute every event for the current simulated time**
  - **Doing this changes system state and may schedule events in the future**
  - **When there are no events left at the current time instance, advance simulated time soonest event in the queue**




# Four-valued Data

- Verilog's nets and registers hold four-valued data
- 0, 1
  - Obvious
- Z
  - Output of an undriven tri-state driver
  - Models case where nothing is setting a wire's value
- X
  - Models when the simulator can't decide the value
  - Initial state of registers
  - When a wire is being driven to 0 and 1 simultaneously
  - Output of a gate with Z inputs
 
# Four-valued Logic

- Logical operators work on three-valued logic



	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

← Output 0 if one input is 0

← Output X if both inputs are gibberish

# Structural Modeling

# Nets and Registers

- Wires and registers can be bits, vectors, and arrays

```
wire a;           // Simple wire
tri [15:0] dbus;  // 16-bit tristate bus
tri #(5,4,8) b;   // Wire with delay
reg [-1:4] vec;   // Six-bit register
trireg (small) q; // Wire stores a small charge
integer imem[0:1023]; // Array of 1024 integers
reg [31:0] dcache[0:63]; // A 32-bit memory
```

# Modules and Instances

- Basic structure of a Verilog module:

```
module mymod(output1, output2, ... input1, input2);  
output output1;  
output [3:0] output2;  
input input1;  
input [2:0] input2;  
...  
endmodule
```

Verilog convention  
lists outputs first



# Instantiating a Module

- Instances of

```
module mymod(y, a, b);
```

- look like

```
mymod mm1(y1, a1, b1); // Connect-by-position
```

```
mymod (y2, a1, b1),  
      (y3, a2, b2); // Instance names omitted
```

```
mymod mm2(.a(a2), .b(b2), .y(c2)); // Connect-by-name
```

# Gate-level Primitives

- Verilog provides the following:

<b>and</b>	<b>nand</b>	<b>logical AND/NAND</b>
<b>or</b>	<b>nor</b>	<b>logical OR/NOR</b>
<b>xor</b>	<b>xnor</b>	<b>logical XOR/XNOR</b>
<b>buf</b>	<b>not</b>	<b>buffer/inverter</b>
<b>bufif0</b>	<b>notif0</b>	<b>Tristate with low enable</b>
<b>bifif1</b>	<b>notif1</b>	<b>Tristate with high enable</b>

# Delays on Primitive Instances

- Instances of primitives may include delays

```
buf      b1(a, b);    // Zero delay
buf #3   b2(c, d);    // Delay of 3
buf #(4,5)b3(e, f);  // Rise=4, fall=5
buf #(3:4:5) b4(g, h); // Min-typ-max
```



# User-Defined Primitives

- **Way to define gates and sequential elements using a truth table**
- **Often simulate faster than using expressions, collections of primitive gates, etc.**
- **Gives more control over behavior with X inputs**
- **Most often used for specifying custom gate libraries**

# A Carry Primitive

```
primitive carry(out, a, b, c);
```

```
output out;
```

```
input a, b, c;
```

```
table
```

```
  00? : 0;
```

```
  0?0 : 0;
```

```
  ?00 : 0;
```

```
  11? : 1;
```

```
  1?1 : 1;
```

```
  ?11 : 1;
```

```
endtable
```

```
endprimitive
```

Always have exactly  
one output

Truth table may  
include don't-care (?)  
entries

# A Sequential Primitive

```
Primitive dff( q, clk, data);
output q; reg q;
input clk, data;
table
// clk data q  new-q
(01)  0  : ?  :  0;    // Latch a 0
(01)  1  : ?  :  1;    // Latch a 1
(0x)  1  : 1  :  1;    // Hold when d and q both 1
(0x)  0  : 0  :  0;    // Hold when d and q both 0
(?0)  ?  : ?  :  -;    // Hold when clk falls
?    (??) : ?  :  -;    // Hold when clk stable
endtable
endprimitive
```

# Continuous Assignment

- Another way to describe combinational function
- Convenient for logical or datapath specifications

```
wire [8:0] sum;
```

```
wire [7:0] a, b;
```

```
wire carryin;
```

```
assign sum = a + b + carryin;
```

Define bus widths



Continuous assignment:  
permanently sets the value of sum to be  $a+b+carryin$

Recomputed when a, b, or carryin changes

# Behavioral Modeling

# Initial and Always Blocks

- Basic components for behavioral modeling

**initial**

**begin**

**... imperative statements ...**

**end**

**always**

**begin**

**... imperative statements ...**

**end**

**Runs when simulation starts**

**Terminates when control reaches the end**

**Good for providing stimulus**

**Runs when simulation starts**

**Restarts when control reaches the end**

**Good for modeling/specifying hardware**

# Initial and Always

- Run until they encounter a delay

**initial begin**

```
#10 a = 1; b = 0;
```

```
#10 a = 0; b = 1;
```

**end**

- or a wait for an event

```
always @(posedge clk) q = d;
```

```
always begin wait(i); a = 0; wait(~i); a = 1; end
```

# Procedural Assignment

- Inside an initial or always block:

```
sum = a + b + cin;
```

- Just like in C: RHS evaluated and assigned to LHS before next statement executes
- RHS may contain wires and regs
  - Two possible sources for data
- LHS must be a reg
  - Primitives or cont. assignment may set wire values



# Imperative Statements

```
if (select == 1)  y = a;  
else             y = b;
```

```
case (op)  
  2'b00: y = a + b;  
  2'b01: y = a - b;  
  2'b10: y = a ^ b;  
  default: y = 'hxxxx;  
endcase
```

# For Loops

- A increasing sequence of values on an output

```
reg [3:0] i, output;
```

```
for ( i = 0 ; i <= 15 ; i = i + 1 ) begin
```

```
    output = i;
```

```
    #10;
```

```
end
```

# While Loops

- A increasing sequence of values on an output

```
reg [3:0] i, output;
```

```
i = 0;
```

```
while (i <= 15) begin
```

```
    output = i;
```

```
    #10 i = i + 1;
```

```
end
```

# Modeling A Flip-Flop With Always

- Very basic: an edge-sensitive flip-flop

```
reg q;
```

```
always @(posedge clk)
```

```
    q = d;
```

- **q = d assignment runs when clock rises: exactly the behavior you expect**

# Blocking vs. Nonblocking

- Verilog has two types of procedural assignment
- Fundamental problem:
  - In a synchronous system, all flip-flops sample simultaneously
  - In Verilog, always @(posedge clk) blocks run in some undefined sequence

# A Flawed Shift Register

- This doesn't work as you'd expect:

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d2 = d1;
```

```
always @(posedge clk) d3 = d2;
```

```
always @(posedge clk) d4 = d3;
```

- These run in some order, but you don't know which

# Non-blocking Assignments

- This version does work:

```
reg d1, d2, d3, d4;
```

```
always @(posedge clk) d2 <= d1;
```

```
always @(posedge clk) d3 <= d2;
```

```
always @(posedge clk) d4 <= d3;
```

Nonblocking rule:  
RHS evaluated when  
assignment runs

LHS updated only after  
all events for the current  
instant have run

# Nonblocking Can Behave Oddly

- A sequence of nonblocking assignments don't communicate

a = 1;

b = a;

c = b;

a <= 1;

b <= a;

c <= b;

Blocking assignment:

a = b = c = 1

Nonblocking assignment:

a = 1

b = old value of a

c = old value of b




# Nonblocking Looks Like Latches

- RHS of nonblocking taken from latches
- RHS of blocking taken from wires

```
a = 1;      “  
b = a;  
c = b;      ”
```



```
a <= 1;  
b <= a;  
c <= b;
```

 

# Building Behavioral Models

# Modeling FSMs Behaviorally

- There are many ways to do it:
- Define the next-state logic combinationaly and define the state-holding latches explicitly
- Define the behavior in a single always @(posedge clk) block
- Variations on these themes

# FSM with Combinational Logic

```
module FSM(o, a, b, reset);  
output o;  
reg o;  
input a, b, reset;  
reg [1:0] state, nextState;  
  
always @(a or b or state)  
case (state)  
2'b00: begin  
    nextState = a ? 2'b00 : 2'b01;  
    o = a & b;  
end  
2'b01: begin nextState = 2'b10; o = 0; end  
endcase
```

Output o is declared a reg because it is assigned procedurally, not because it holds state

Combinational block must be sensitive to any change on any of its inputs

(Implies state-holding elements otherwise)

# FSM with Combinational Logic

```
module FSM(o, a, b, reset);
```

```
...
```

```
always @(posedge clk or reset)
```

```
  if (reset)
```

```
    state <= 2'b00;
```

```
  else
```

```
    state <= nextState;
```



Latch implied by sensitivity to the clock or reset only

# FSM from Combinational Logic

```
always @(a or b or state)
case (state)
  2'b00: begin
    nextState = a ? 2'b00 : 2'b01;
    o = a & b;
  end
  2'b01: begin nextState = 2'b10; o = 0; end
endcase
```

This is a Mealy machine because the output is directly affected by any change on the input

```
always @(posedge clk or reset)
if (reset)
  state <= 2'b00;
else
  state <= nextState;
```

# FSM from a Single Always Block

```
module FSM(o, a, b);  
output o; reg o;  
input a, b;  
reg [1:0] state;
```

```
always @(posedge clk or reset)  
if (reset) state <= 2'b00;  
else case (state)  
2'b00: begin  
state <= a ? 2'b00 : 2'b01;  
o <= a & b;  
end  
2'b01: begin state <= 2'b10; o <= 0; end  
endcase
```

Expresses Moore machine behavior:

Outputs are latched

Inputs only sampled at clock edges

Nonblocking assignments used throughout to ensure coherency.


RHS refers to values calculated in previous clock cycle

# Simulating Verilog


 
# How Are Simulators Used?

- Testbench generates stimulus and checks response
- Coupled to model of the system
- Pair is run simultaneously



# Writing Testbenches

```
module test;  
reg a, b, sel;
```

Inputs to device  
under test

```
mux m(y, a, b, sel);
```

Device under test

```
initial begin
```

\$monitor is a built-in  
event driven "printf"

```
    $monitor($time,, "a = %b b=%b sel=%b y=%b",  
             a, b, sel, y);
```

```
    a = 0; b = 0; sel = 0;
```

```
    #10 a = 1;
```

```
    #10 sel = 1;
```

```
    #10 b = 1;
```

```
end
```

Stimulus generated by  
sequence of  
assignments and delays

# Simulation Behavior

- **Scheduled using an event queue**
- **Non-preemptive, no priorities**
- **A process must explicitly request a context switch**
- **Events at a particular time unordered**
  
- **Scheduler runs each event at the current time, possibly scheduling more as a result**

# Two Types of Events

- Evaluation events compute functions of inputs
- Update events change outputs
- Split necessary for delays, nonblocking assignments, etc.

Update event  
writes new value  
of a and  
schedules any  
evaluation events  
that are sensitive  
to a change on a

$$a \leq b + c$$

Evaluation event  
reads values of b and  
c, adds them, and  
schedules an update  
event

# Simulation Behavior

- **Concurrent processes (initial, always) run until they stop at one of the following**
- **#42**
  - **Schedule process to resume 42 time units from now**
- **wait(cf & of)**
  - **Resume when expression “cf & of” becomes true**
- **@(a or b or y)**
  - **Resume when a, b, or y changes**
- **@(posedge clk)**
  - **Resume when clk changes from 0 to 1**

# Simulation Behavior

- Infinite loops are possible and the simulator does not check for them
- This runs forever: no context switch allowed, so ready can never change

```
while (~ready)
    count = count + 1;
```

- Instead, use

```
wait(ready);
```

# Simulation Behavior

- Race conditions abound in Verilog
- These can execute in either order: final value of a undefined:

```
always @(posedge clk) a = 0;
```

```
always @(posedge clk) a = 1;
```

# Simulation Behavior

- **Semantics of the language closely tied to simulator implementation**
- **Context switching behavior convenient for simulation, not always best way to model**
- **Undefined execution order convenient for implementing event queue**



# Verilog and Logic Synthesis

# Logic Synthesis

- **Verilog is used in two ways**
  - **Model for discrete-event simulation**
  - **Specification for a logic synthesis system**
- **Logic synthesis converts a subset of the Verilog language into an efficient netlist**
- **One of the major breakthroughs in designing logic chips in the last 20 years**
- **Most chips are designed using at least some logic synthesis**

# Logic Synthesis

- Takes place in two stages:
- Translation of Verilog (or VHDL) source to a netlist
  - Register inference
- Optimization of the resulting netlist to improve speed and area
  - Most critical part of the process
  - Algorithms very complicated and beyond the scope of this class: Take Prof. Nowick's class for details

# Translating Verilog into Gates

- **Parts of the language easy to translate**
  - **Structural descriptions with primitives**
    - **Already a netlist**
  - **Continuous assignment**
    - **Expressions turn into little datapaths**
- **Behavioral statements the bigger challenge**

# What Can Be Translated

- **Structural definitions**
  - Everything
- **Behavioral blocks**
  - Depends on sensitivity list
  - Only when they have reasonable interpretation as combinational logic, edge, or level-sensitive latches
  - Blocks sensitive to both edges of the clock, changes on unrelated signals, changing sensitivity lists, etc. cannot be synthesized
- **User-defined primitives**
  - Primitives defined with truth tables
  - Some sequential UDPs can't be translated (not latches or flip-flops)

# What Isn't Translated

- **Initial blocks**
  - Used to set up initial state or describe finite testbench stimuli
  - Don't have obvious hardware component
- **Delays**
  - May be in the Verilog source, but are simply ignored
- **A variety of other obscure language features**
  - In general, things heavily dependent on discrete-event simulation semantics
  - Certain “disable” statements
  - Pure events

# Register Inference

- **The main trick**
- **reg does not always equal latch**
- **Rule: Combinational if outputs always depend exclusively on sensitivity list**
- **Sequential if outputs may also depend on previous values**

# Register Inference

- **Combinational:**

```
reg y;  
always @(a or b or sel)  
  if (sel) y = a;  
  else y = b;
```

Sensitive to changes  
on all of the variables  
it reads

Y is always assigned

- **Sequential:**

```
reg q;  
always @(d or clk)  
  if (clk) q = d;
```

q only assigned when  
clk is 1



# Register Inference

- A common mistake is not completely specifying a case statement
- This implies a latch:

```
always @(a or b)
```

```
case ({a, b})
```


```
  2'b00 : f = 0;
```

```
  2'b01 : f = 1;
```

```
  2'b10 : f = 1;
```

```
endcase
```

f is not assigned  
when {a,b} = 2b'11

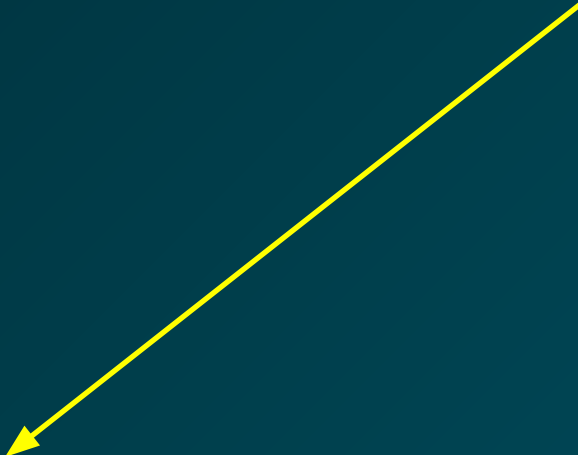

# Register Inference

- The solution is to always have a default case

```
always @(a or b)
```

```
case ({a, b})
```

```
  2'b00: f = 0;
```

```
  2'b01: f = 1;
```

```
  2'b10: f = 1;
```

```
  default: f = 0;
```

```
endcase
```

f is always assigned



# Inferring Latches with Reset

- Latches and Flip-flops often have reset inputs
- Can be synchronous or asynchronous
- Asynchronous positive reset:

```
always @(posedge clk or posedge reset)
```

```
  if (reset)
```

```
    q <= 0;
```

```
  else q <= d;
```

# Simulation-synthesis Mismatches

- Many possible sources of conflict
- Synthesis ignores delays (e.g., #10), but simulation behavior can be affected by them
- Simulator models X explicitly, synthesis doesn't
- Behaviors resulting from shared-variable-like behavior of regs is not synthesized
  - always `@(posedge clk) a = 1;`
  - New value of a may be seen by other `@(posedge clk)` statements in simulation, never in synthesis

# Compared to VHDL

- Verilog and VHDL are comparable languages
- VHDL has a slightly wider scope
  - System-level modeling
  - Exposes even more discrete-event machinery
- VHDL is better-behaved
  - Fewer sources of nondeterminism (e.g., no shared variables)
- VHDL is harder to simulate quickly
- VHDL has fewer built-in facilities for hardware modeling
- VHDL is a much more verbose language
  - Most examples don't fit on slides